

Name : Mahardhika Bathiarto Dim Zarita

Class : X

NIM :L200184134

Practice 1

1. Make a circuit of image and edit the everything properties of component as showed of table.


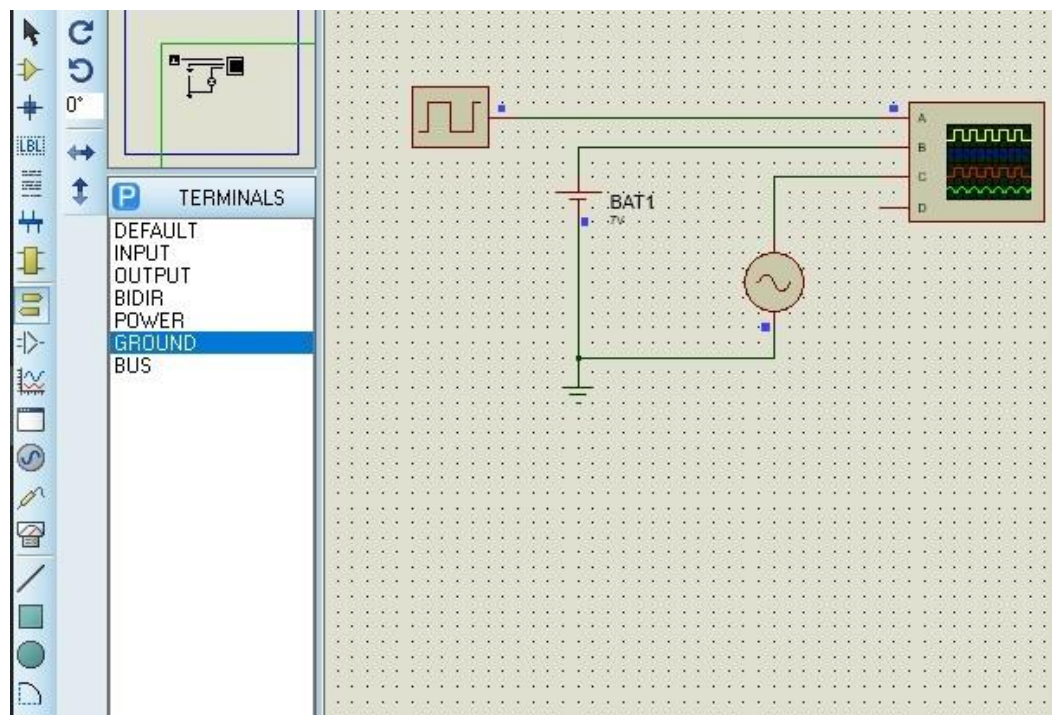


Table 1. component of circuit

No	Device	Information
1	Alternator	$V = 5 \text{ Volt}$, $f = 100 \text{ Hz}$
2	Cell	$V = 5 \text{ Volt}$
3	Clock	$F = 100 \text{ Hz}$
4	Ground	Pick from Terminals
5	Osiloskop	Pick from Instrument

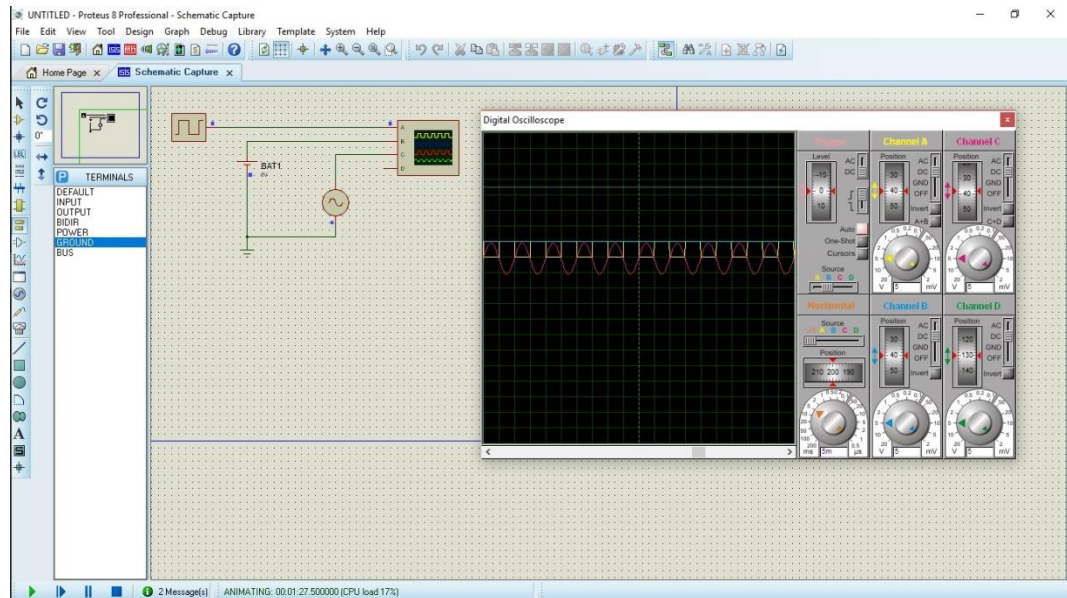- The simulation will show to us a signal line from batre,clock and alternator.



And explain it !


→ Channel A is **clock**, the shape of channel A is square. it is analog signal. Channel B is **Cell**, the shape of channel B is line, it is digital signal. Channel C is **Alternator**, the shape of channel C is warped, it is analog signal. The channel D is **nothing**.

- Turn off that simulation ! then edit your component as table 2.

Table 2. Properties component

No	Device	Information
1	Alternator	V = 10 Volt, f = 50 Hz
2	Cell	V = 7 Volt
3	Clock	F = 200 Hz

4. Run the simulation !

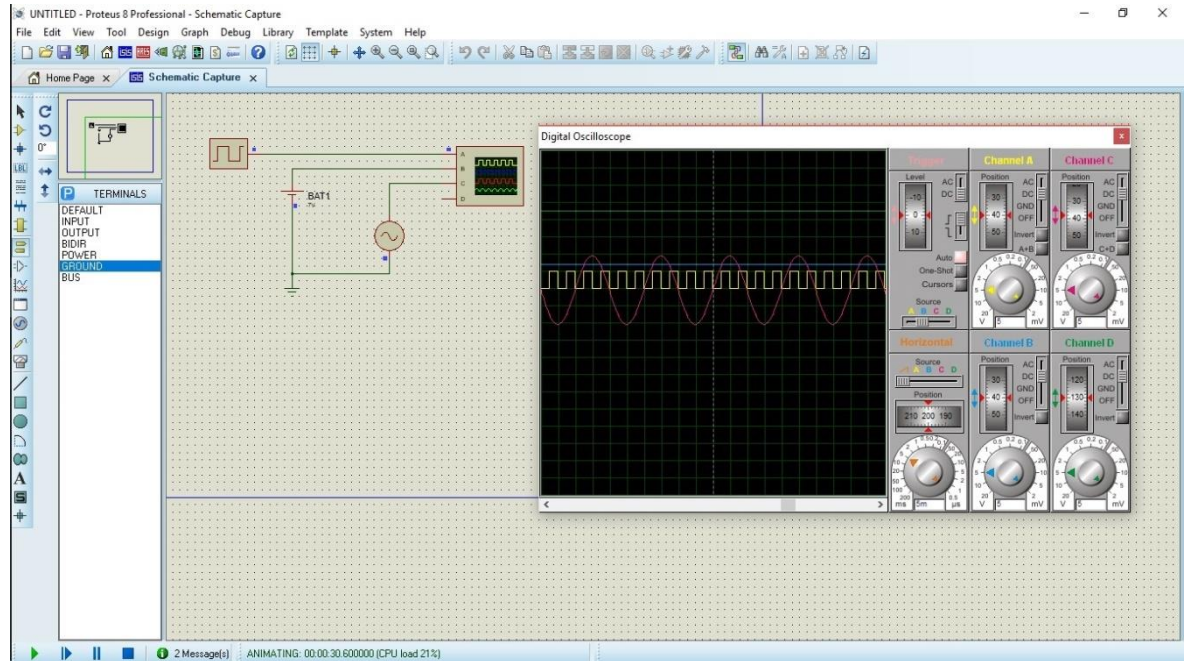

And explain it !

→ Trigger on source B, Channel A is square, the length of A is 1.5. Channel B is line, channel C is warped, it is so big size.

5. Answer The Questions !

- a. What is the different between analog signal and digital !

The shape for analog is line, and digital is square/warped

- b. How about the signal characteristic of every component !

1. Signal by Alternator :

→ Analog, warped shape

2. Signal by Battery :

→ Analog, line shape

3. Signal by clock source :

→ Digital, square shape

- c. Make the conclusion from your observation of kind exercise of signal.

→ If the shape is square, it is digital. If the shape is line and warped, it is analog signal.

Practice 2

1. Make a circuit Proteus 8 simulation on this image.


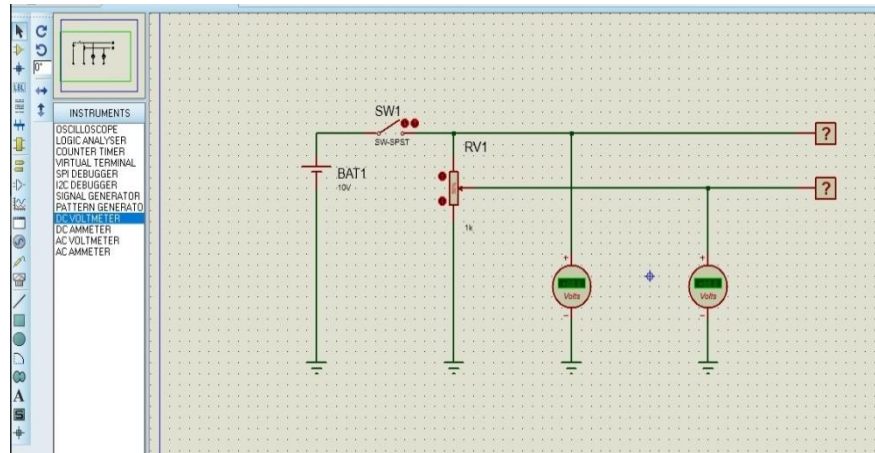


Table 3.component for circuit.

No	Device	Information
1	Cell	Edit to 10 volt
2	SW-SPT	
3	POT-HG	
4	Logicprobe	
5	Ground	Pick from Terminals
6	DC Voltmeter	Pick from Instrument

2. Run that simulation as image!

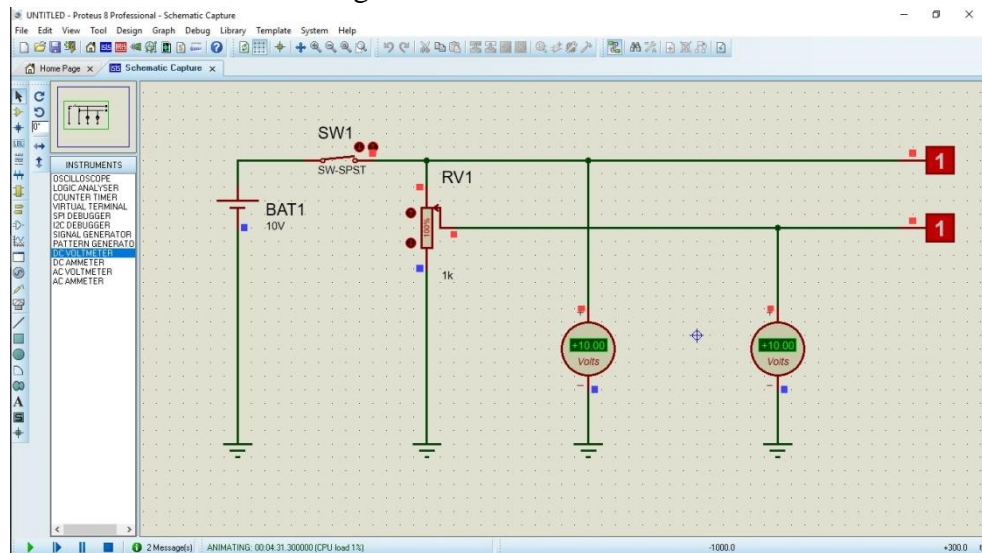

3. Click SW1 ! in your simulation, answer the question !
 - a. Voltmeter DC 1 : +10.00 Volt

- b. Voltmeter DC 2 : +5.00 Volt
 - c. Logicprobe 1 show logic condition : 1
 - d. Logicprobe 2 show logic condition : 1
4. Click RV1 component (Resistor Variabel/POT-HG) up and down ! and then answer the question !
- a. Logicprobe 2 show logic condition 1(**HIGH**)
If Voltmeter DC 2 : +5.00 Volts until +10.00 Volts
 - b. Logicprobe 2 menunjukan kondisi logika 0 (Low)
If Voltmeter DC 2 : +00.00 Volts until +02.00 Volts
5. Make a conclusion based of your analys in range signal digital exercise !
- ➔ If voltmeter DC 1 is high until +10.00,the value of logicprobe is 1. And if the Voltmeter is low until +00.00 until +02.00 the value of logicprobe is 0.